

1.

$$a. = xyz + x'y + xyz'$$

$$= xy(z + z') + x'y$$

$$= xy + x'y$$

$$= y(x + x')$$

$$\boxed{= y}$$

$$\text{b. } = (x+y)^1 \cdot (x^1 + y^1)$$

$$= x^1 y^1 \cdot (x^1 + y^1)$$

$$= x^1 x^1 y^1 + x^1 y^1 y^1$$

$$= x^1 y^1 + x^1 y^1$$

$$= \boxed{x^1 y^1}$$

$$L = A'C' + ABC + AC'$$

 $\approx$ 

$$= C'(A' + A) + ABC$$

$$= C' + ABC$$

$$= C' + AB$$

$$d. \quad = (A+B)^I \cdot (A^I + B^I)^I$$

$$= A^I B^I \cdot AB$$

$$= A^I B^I AB$$

$$= F$$

2.

$$\text{a. } \begin{array}{l} \begin{array}{|c|c|c|c|c|} \hline A & B & C & D & F(A, B, C, D) \\ \hline 0 & 0 & 0 & 0 & 1 \\ \hline 0 & 0 & 0 & 1 & 0 \\ \hline 0 & 0 & 1 & 0 & 1 \\ \hline 0 & 0 & 1 & 1 & 0 \\ \hline 0 & 1 & 0 & 0 & 0 \\ \hline 0 & 1 & 1 & 0 & 0 \\ \hline 0 & 1 & 0 & 1 & 1 \\ \hline 0 & 1 & 1 & 1 & 1 \\ \hline 1 & 0 & 0 & 0 & 1 \\ \hline 1 & 0 & 0 & 1 & 0 \\ \hline 1 & 0 & 1 & 0 & 1 \\ \hline 1 & 0 & 1 & 1 & 0 \\ \hline 1 & 1 & 0 & 0 & 1 \\ \hline 1 & 1 & 1 & 0 & 0 \\ \hline \end{array} & ab \setminus cd \\ \hline \end{array}$$

00	1	00	1	01	0	11	1	10	0
01	0	01	0	11	1	00	0	01	0
10	0	10	0	10	1	00	0	00	1
11	1	11	1	10	0	00	1	00	0
10	0	10	0	01	1	00	0	00	1

$$F = A'B'D + ABC' + B'D'$$

$$\text{b. } F(A, B, C) = (A + B + C)' + (ABC') + B'C$$

A	B	C		F(A, B, C)
0	0	0		1
0	0	1		1
0	1	0		0
0	1	1		0
1	0	0		0
1	0	1		1
1	1	0		1
1	1	1		0

A \ BC	00	01	11	10
0	1	1	0	0
1	0	1	1	1

$$F = A'B' + B'C + ABC'$$

$$C. \quad F(A, B, C, D, E) = A'BCE' + A'CE' + AC'D + AE + DE$$

A B C D E	F(A, B, C, D, E)
0 0 0 0 0	0
0 0 0 0 1	0
0 0 0 1 0	0
0 0 0 1 1	1
0 0 1 0 0	1
0 0 1 0 1	0
0 0 1 1 0	1
0 0 1 1 1	1
0 1 0 0 0	0
0 1 0 0 1	0
0 1 0 1 0	0
0 1 0 1 1	1
0 1 1 0 0	1
0 1 1 0 1	0
0 1 1 1 0	1
0 1 1 1 1	1

Continued...

A	B	C	D	E	$F(A, B, C, D, E)$
1	0	0	0	0	0
1	0	0	0	1	1
1	0	0	1	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	1
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	0
1	1	0	0	1	1
1	1	0	1	0	1
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	0	1	1
1	1	1	1	0	0
1	1	1	1	1	1

ABC \ DE    00    01    11    10

000	0	0	1	0
001	1	0	1	1
011	1	0	1	1
010	0	0	1	0
100	0	1	1	1
101	0	1	1	0
111	0	1	1	1
110	0	1	1	0

$$F = DE + AE + A'C'E' + A'C'D$$

In	ABC	Output					
		01	02	03	04	05	06
000		0	0	0	0	0	0
001		0	0	0	0	0	1
010		0	0	0	1	0	0
011		0	0	1	0	0	1
100		0	1	0	0	0	0
101		0	1	1	0	0	1
111		1	1	0	0	0	1
110		1	0	0	1	0	0

3. Bit 6:

$\text{IN}$	$\text{AB}$	$C$	0	1
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	0	0	0

$$F = AB$$

$\text{IN}$	$\text{AB}$	$C$	0	1
00	0	0	0	0
01	0	0	0	0
11	0	0	0	1
10	1	1	1	1

Bit 5:

$$F = AB' + AC$$

Bit 4:

$\text{AB}$	$C$	0	1
00	0	0	0
01	0	0	1
11	0	0	0
10	0	1	1

$$F = A'B'C + AB'C$$

Bit 3:

$\text{AB}$	$C$	0	1
00	0	0	0
01	0	1	0
11	0	0	0
10	0	0	0


$$F = BC'$$

		Bit 2:				Bit 1:	
		A	B	C	A	B	C
00	0	0	0	0	00	0	0
01	0	0	0	1	01	0	1
11	0	0	1	1	11	0	1
10	0	0	1	0	10	0	1

$$F = 0$$

$$F = C$$


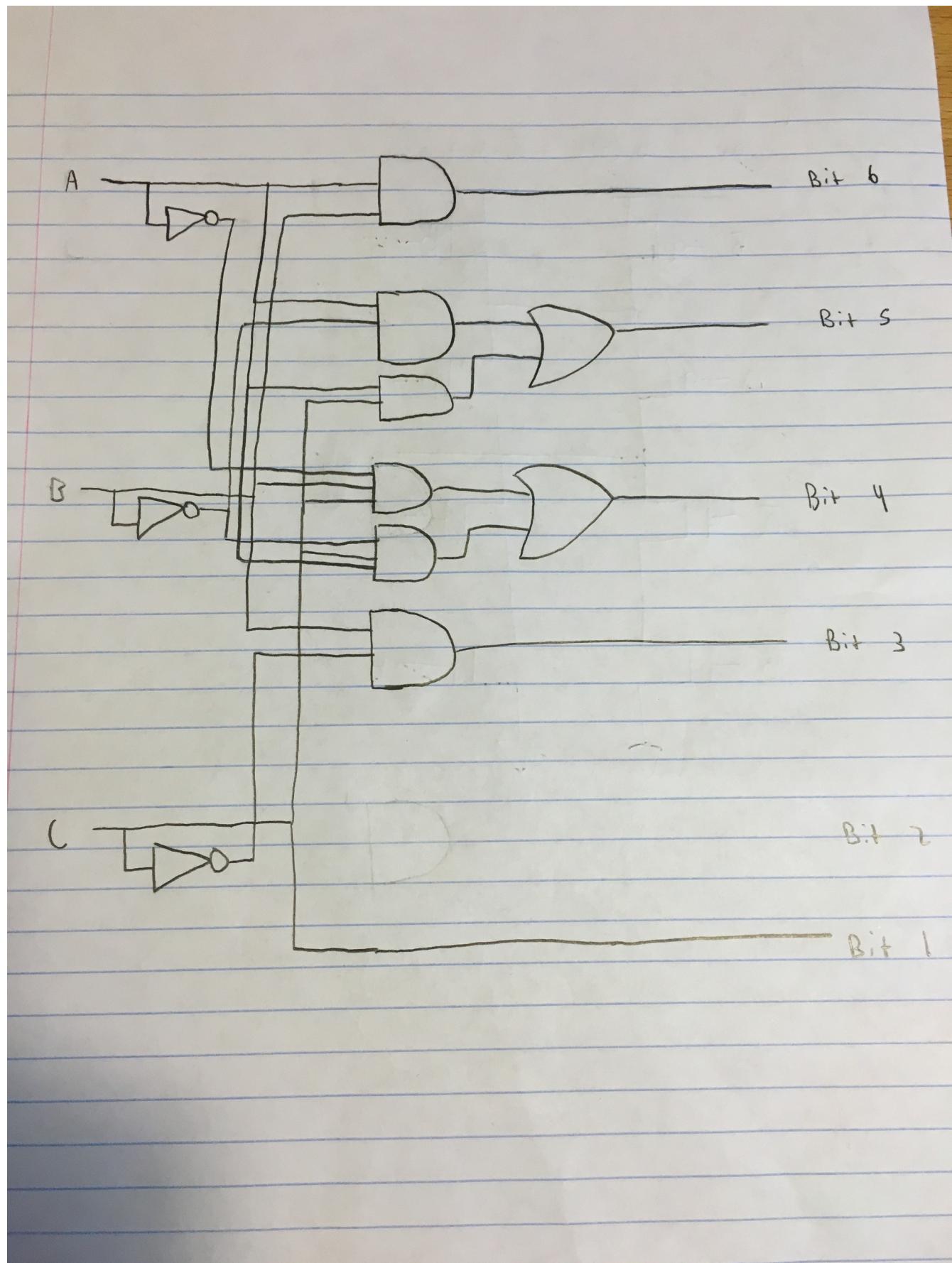
$$F = AB + AB' + AC + A'BC + AB'C + B'C + C$$



a.


4.

A

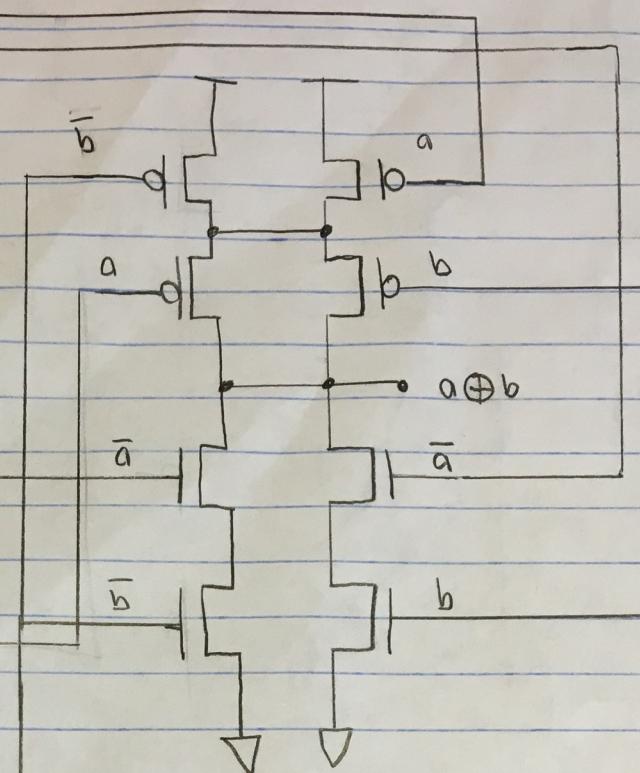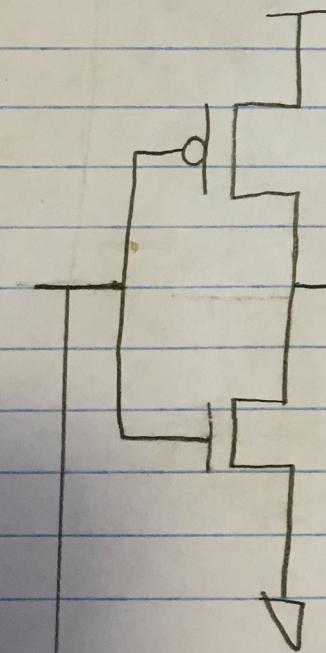



B


b.

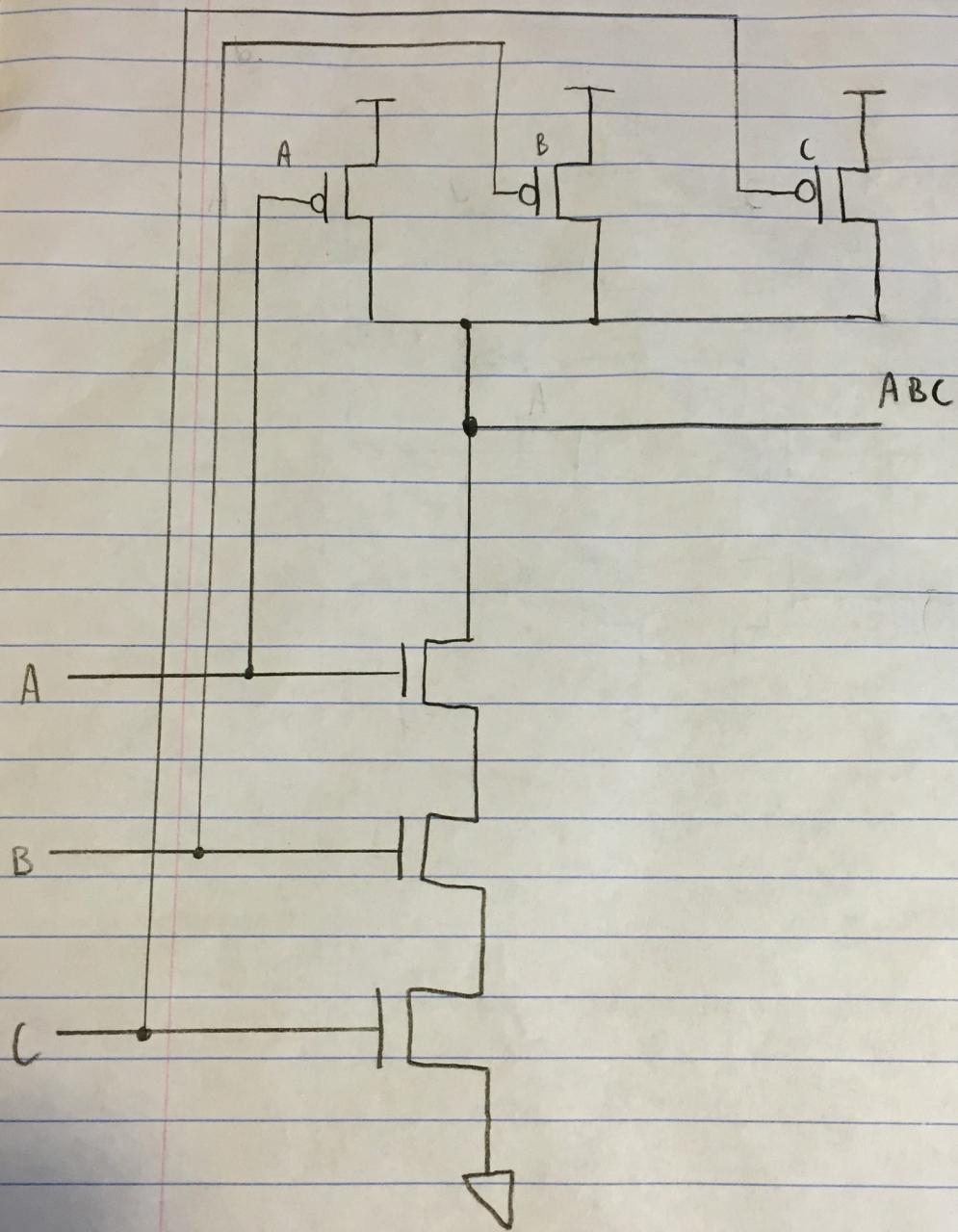


c.

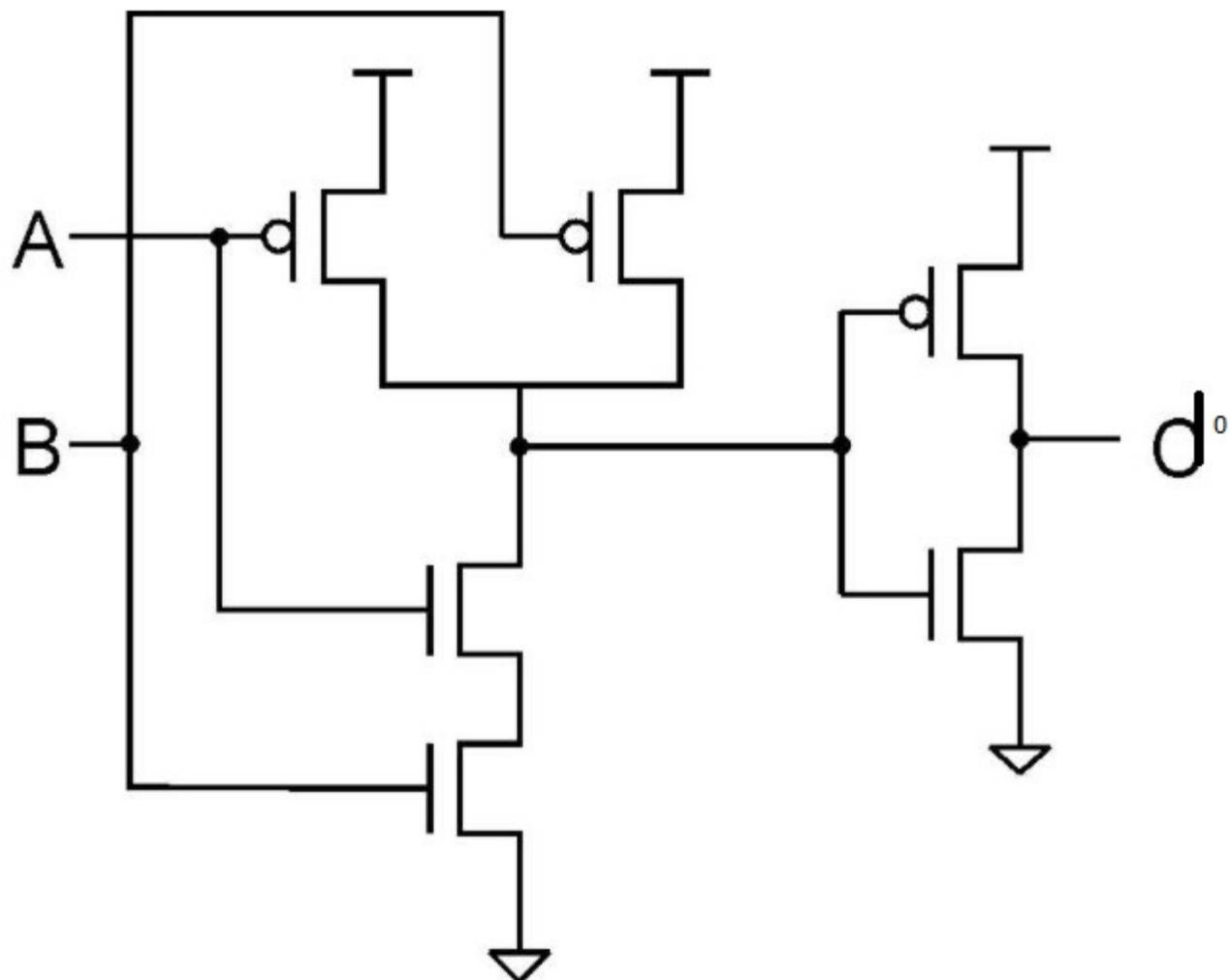


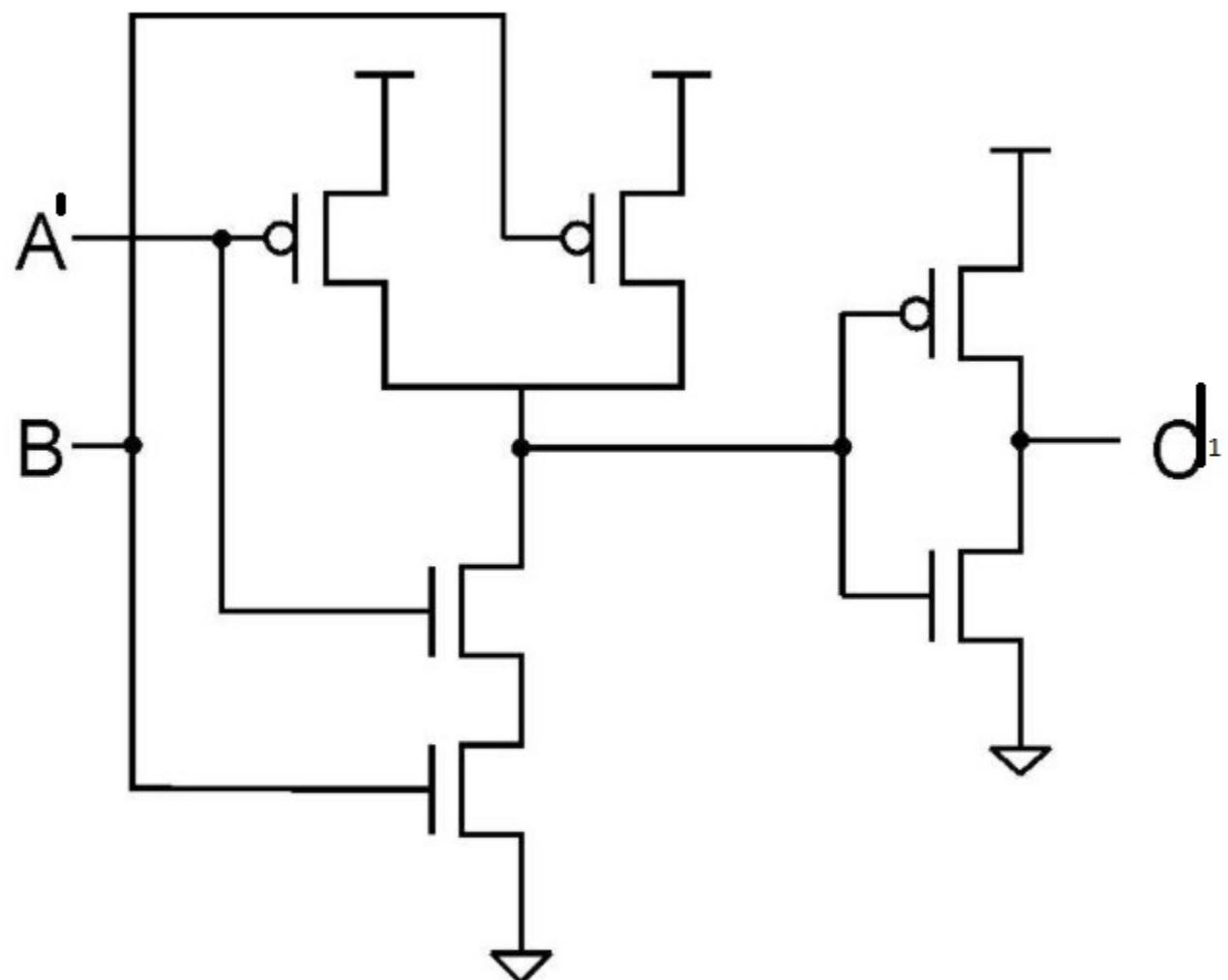

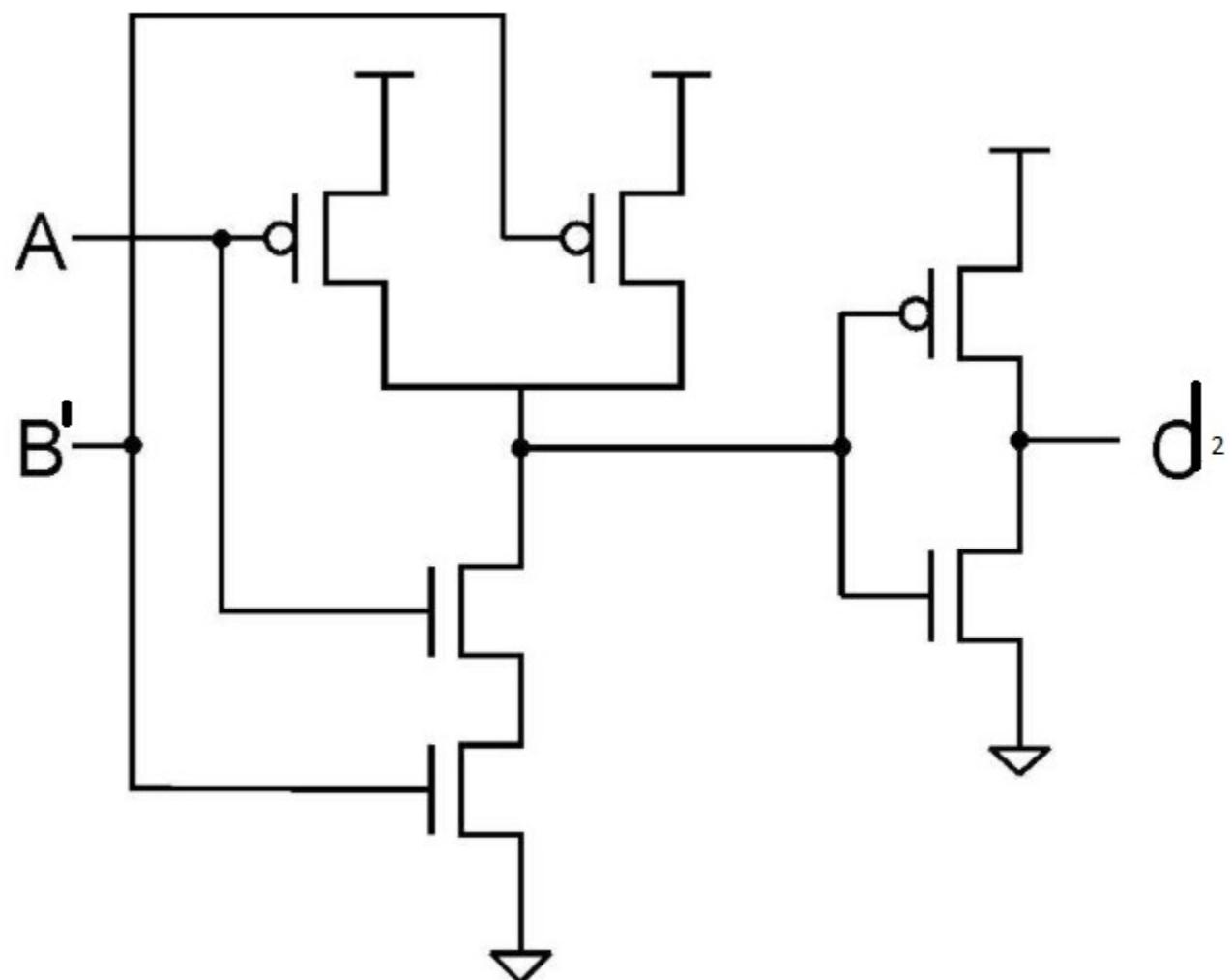

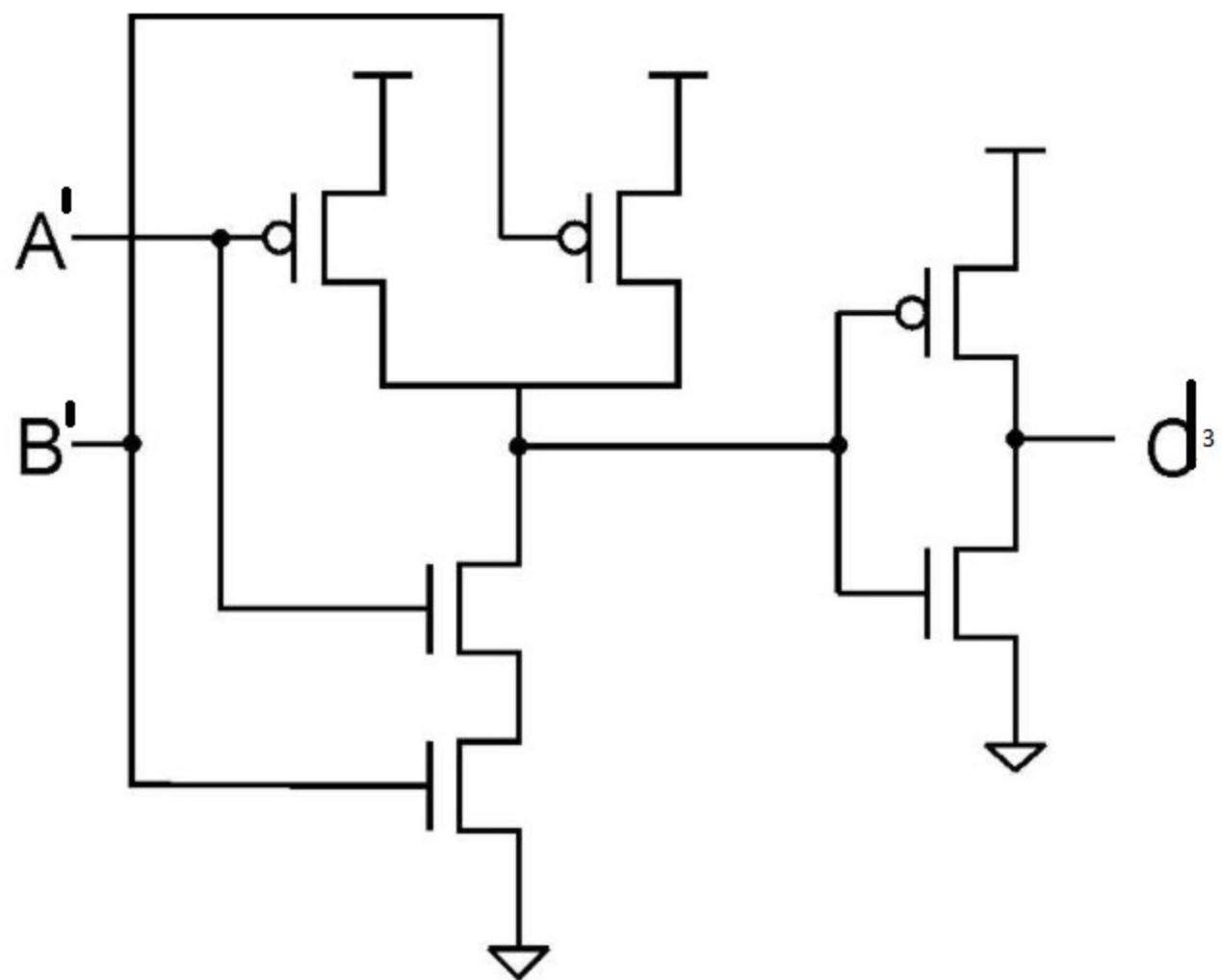


d.

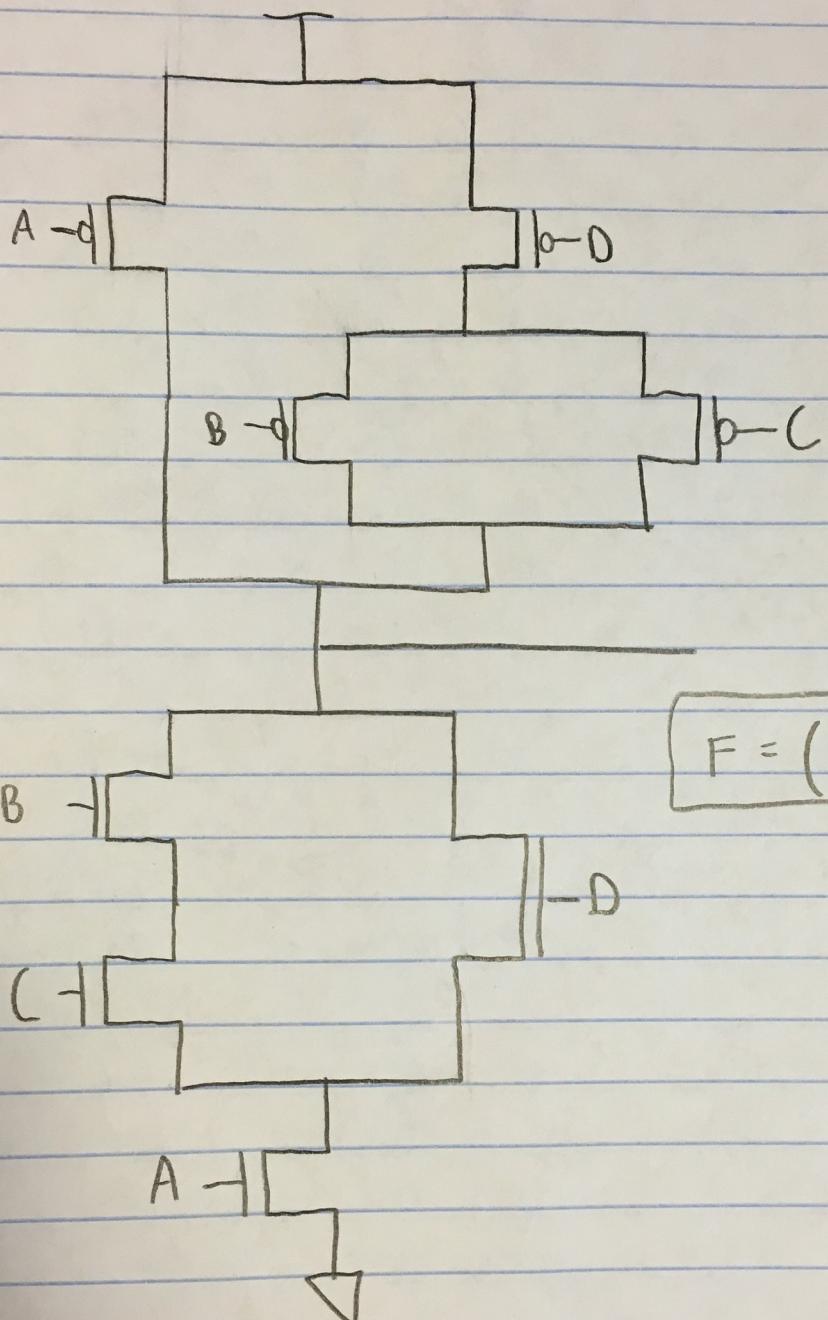

$$F = (A(B+C'D))'$$

5.

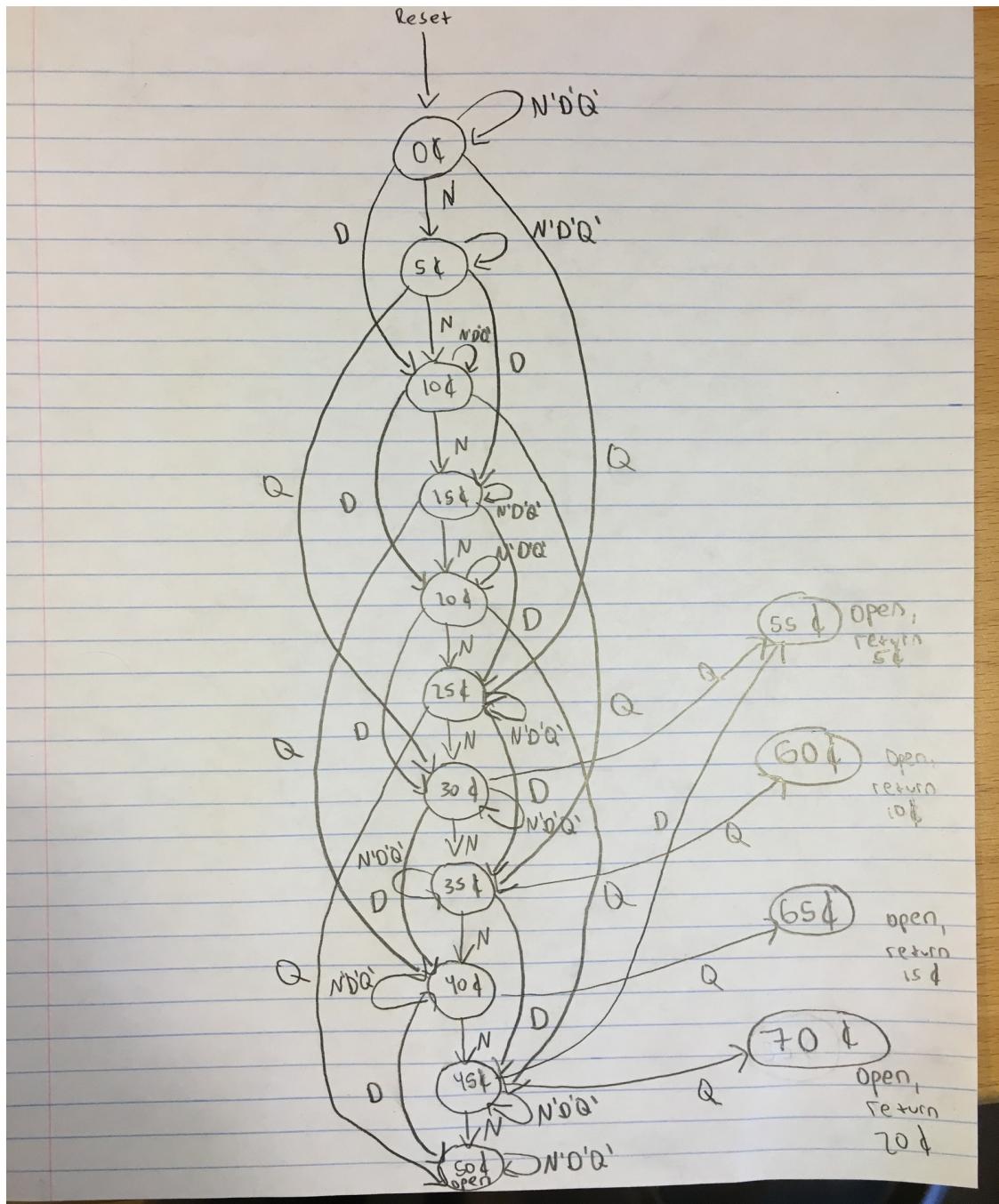

I designed it to be a Moore state diagram. The output is associated with the state. In this case, it is not associated with transitions or the inputs. One could have made the decision to express it in such a way, however. If it is in the state 50, 55, 60, 65, or 70C then the signal OPEN is set.


6.

a.

$$b. D_A = x'A + xY$$

$$D_B = x'A + xY$$

$$\bar{z} = XB$$

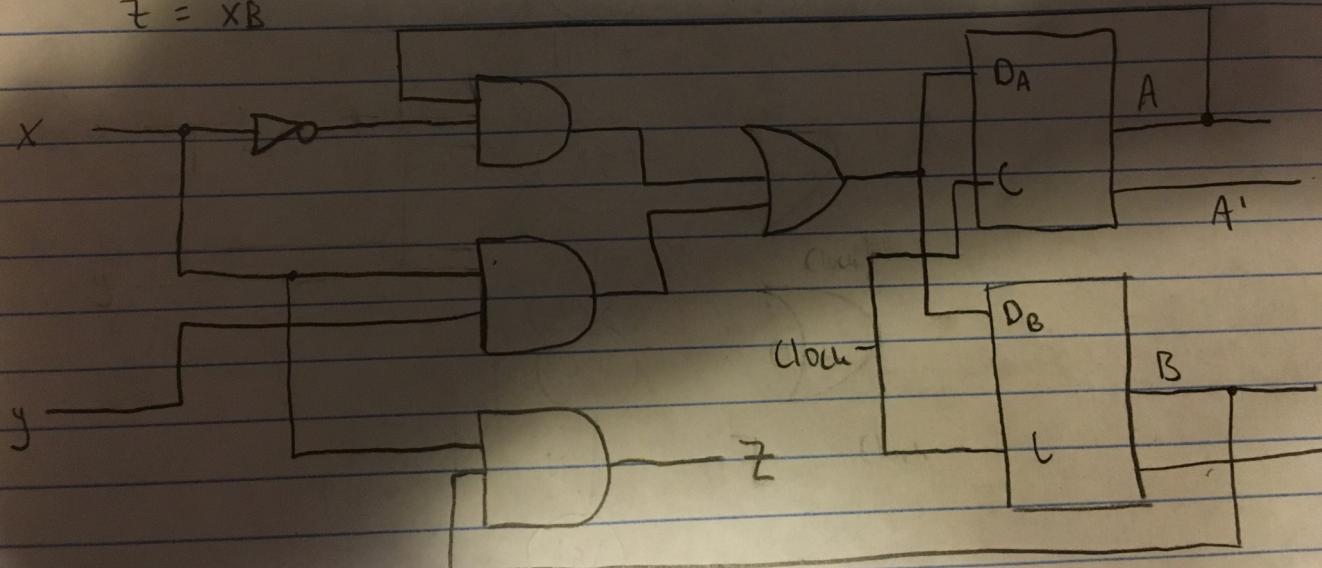

Present State		Inputs		Next State		Output
A	B	X	Y	A	B	z
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	1	1	0
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	0	0	1
0	1	1	1	1	1	1

1	0	0	0	1	1	0
1	0	0	1	1	1	0
1	0	1	0	0	0	0
1	0	1	1	1	1	0
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	0	0	1
1	1	1	1	1	1	1

